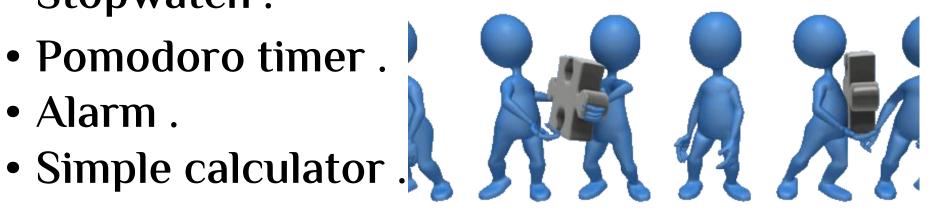


Team members


- Nada Elsayed Arafat sec:8
- Nahla Hatem Mohamed sec:8
- Wafaa Samy
 sec:8
- Mona Khaled Sobhy sec:8
- Mona Elsayed Ismail sec:8
- Haidy Ashraf
 sec:8
- Heba Mohamed (leader) sec:8



- Digital watch.
- Date .
- Stopwatch.
- Pomodoro timer.
- Alarm.




Semi Smart Watch

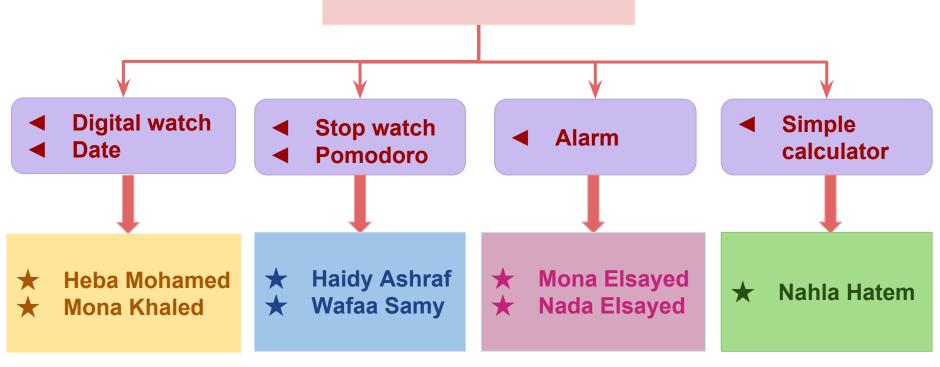

Semi Smart Watch diagram

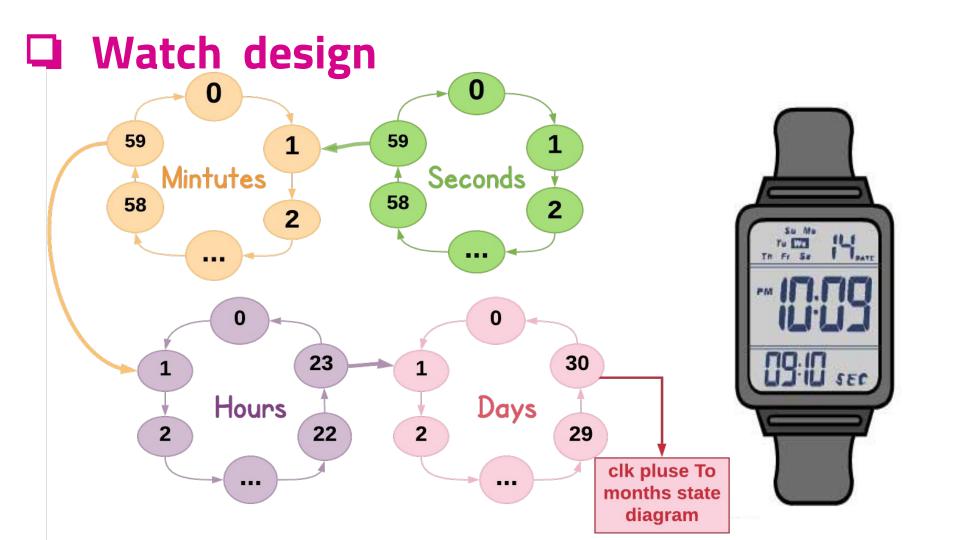- Contains five buttons to move different parts
- StopWatch_on: for starting Stopwatch.
- StopWatch_off: to stop Stopwatch.
- Pomodro_in : to run pomodoro timer.
- Alarm_in : to Turn on the alarm clock.



Data

what date depend on?

it depends on the watch.

How that work?

- When digital watch became [23:59:59] the days counter +1.
- days counter start from (1).
- months counter start from (1).
- years counter start from (2018).
- The year contains several months:-
- 24 7 5 35 41

 Months Days Hours Minutes Seconds
- Months have 30 days: April, June, September, November.
- Months have 31 days: January, March, May, July, August, October, December.
- and February has 28 days .


And so...


when it became [31/12/2018] the counter of years +1.

Date design

Note:-

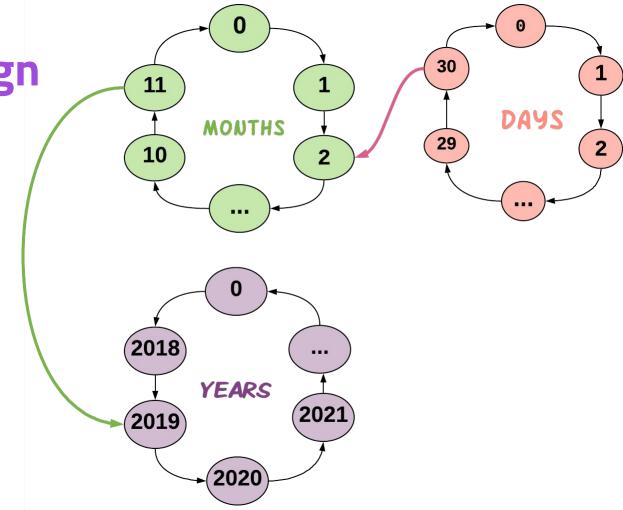- zero stateoccurs whenyou press theRST button
- the initial value of Date is [1/1/2018]



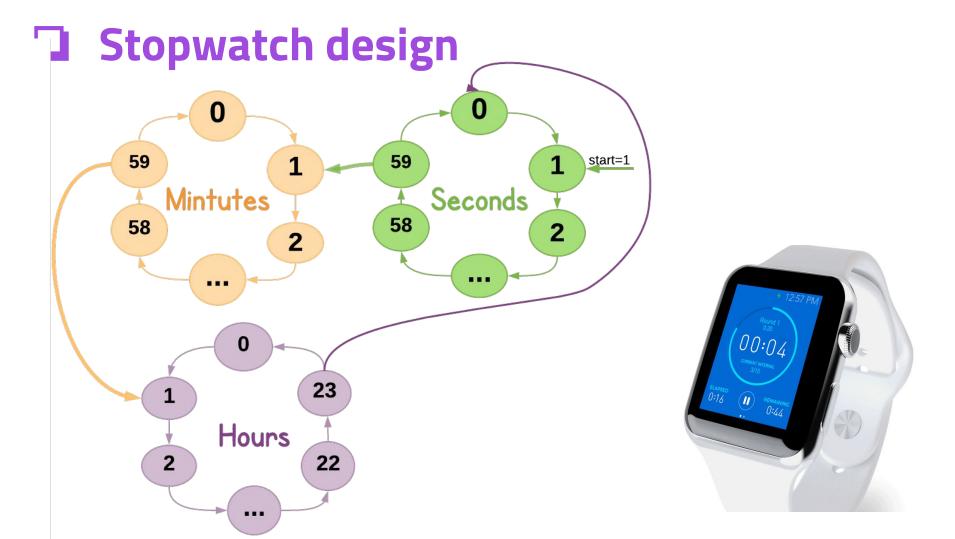

Pomodoro technique

What is the pomodoro and how does it operate?


- the pomodoro in English of the Italian word means (tomato).
- The technique uses a timer to break down work into intervals, traditionally 25 minutes in length, separated by short breaks traditionally 5 minutes in length.

How the program in VHDL works?

- when pressing GO:
 The pomodoro starts to count from 0 to 25 minutes (study).
 and then it will count from 0 to 5 minutes (break).
 another press it will count from 0 to 25 minutes (study).
- Contains input "GO" to control states.



Pomodoro design

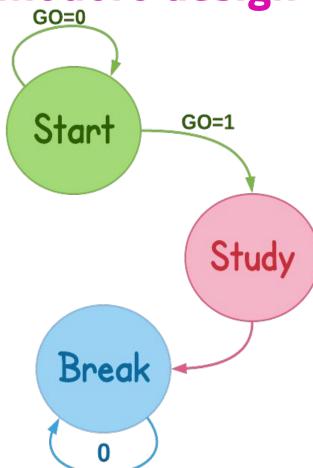


□ Alarm

- inputs
 - alarm_armed : To set the alarm .
- outputs
 - buzzz: A voice occurs to wake up.
- States
 - Off : Alarm clock is closed.
 - armed: the alarm clock is set and waiting for the
 - right time to move to its wakeup state.
 - wake up: The alarm clock sounds buzzz.



Alarm design

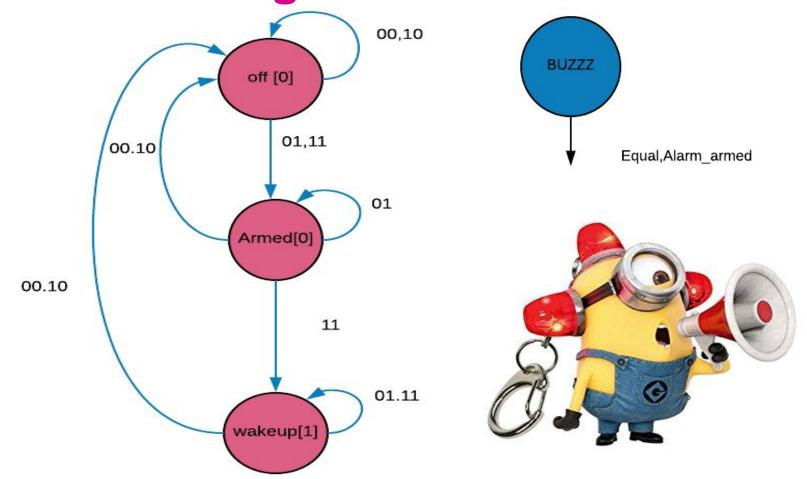

□ Simple calculator

Operations

The calculator contains four basic operations:-

- Addition
- Subtraction
- Multiplication
- Division

Each operation has block that is responsible for its execution




Inputs

- we have 2 input(first and second number) where.
- each input consists of 8-bit and button to control it one of the two buttons is for single numbers and the other for the dozens number
- each button connected to counter when the user push the button the value of it until it reach the value desired by the user.

Outputs

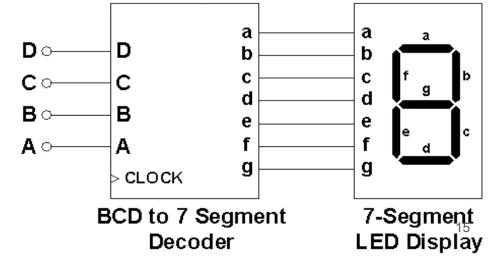the output appears to user on the seven segment by using decoder



the control block

Used for controlling The type of process when pressing the multiplication button (for example) the output is the multiply of the two numbers .

Note:

- if the user active two operations, for example it is multiplying and addition, then the machine calculates one operation according to priority.
- The priority of addition > subtraction > multiplication > division .

□ Simple Calculator design

